



## ECE 545—Digital System Design with VHDL Lecture 4

Algorithmic State Machines and Dataflow  
VHDL Coding

9/16/08

1

### Outline

- Algorithmic State Machines
  - Sorting Example
- Dataflow VHDL (for combinational logic)
- Arithmetic using `std_logic_arith`

2

## Resources

- Volnei A. Pedroni, *Circuit Design with VHDL*
  - **Chapter 5, Concurrent Code**
  - **Chapter 4.1, Operators**
- Stephen Brown and Zvonko Vranesic, *Fundamentals of Digital Logic with VHDL Design, 2<sup>nd</sup> or 3<sup>rd</sup> Edition*
  - **Chapter 8.10 Algorithmic State Machine (ASM) Charts**
  - **Chapter 10.2.1 A Bit-Counting Circuit**
  - **Chapter 10.2.2 ASM Chart Implied Timing Information**
  - **Chapter 10.2.6 Sort Operation**  
(handouts distributed in class)

3


## Algorithmic State Machines

4

## Algorithmic State Machines

- We will continue to work through the Sorting Example from last week's lecture

5

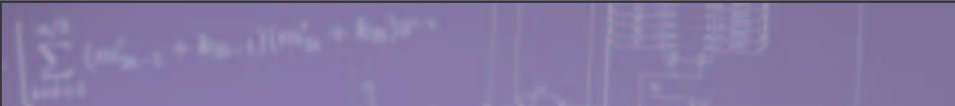

## Describing Combinational Logic Using Dataflow VHDL


6

## Brief Class Review

- In this class we have covered the following items **without using VHDL:**
  - Gates and combinational logic blocks (Lecture 2)
  - Sequential logic blocks (Lecture 3)
  - State machines (Lecture 3)
  - Algorithmic state machines (Lectures 3 & 4)
- Now we will learn how to code these blocks in VHDL


7
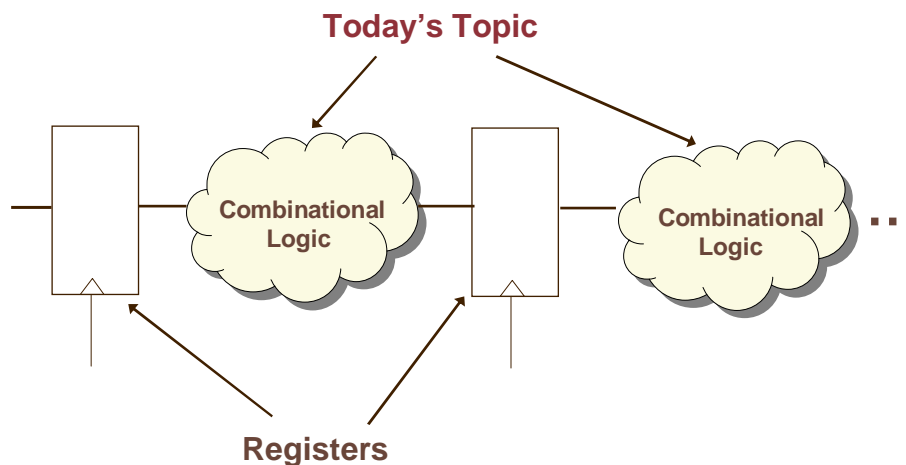
## Register Transfer Level (RTL) Design Description



8

## VHDL Design Styles (Architecture)

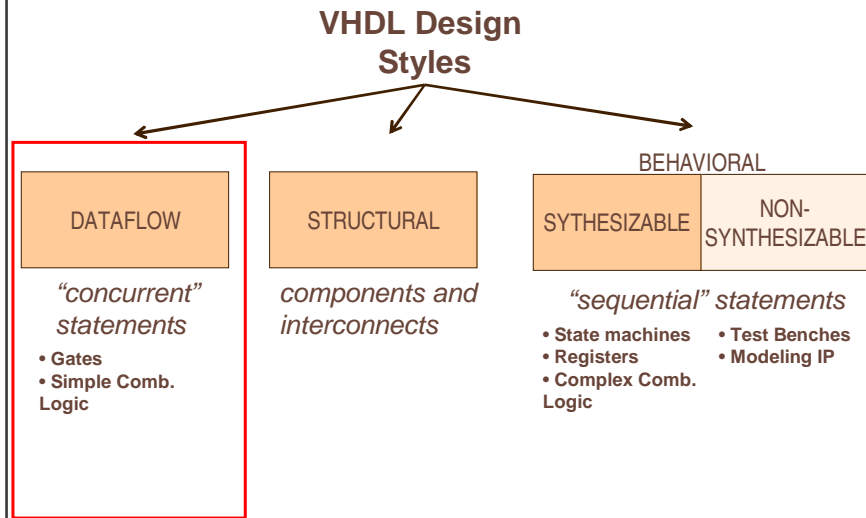

9

## Dataflow VHDL

### *Major instructions*

#### **Concurrent statements**

- concurrent signal assignment ( $\Leftarrow$ )
- conditional concurrent signal assignment  
(when-else)
- selected concurrent signal assignment  
(with-select-when)
- generate scheme for equations  
(for-generate)

10

# Dataflow VHDL

## Major instructions

### Concurrent statements

- **concurrent signal assignment** ( $\Leftarrow$ )
- conditional concurrent signal assignment  
(when-else)
- selected concurrent signal assignment  
(with-select-when)
- generate scheme for equations  
(for-generate)

# Dataflow VHDL: Full Adder

$c_i$	$x_i$	$y_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table


$c_i \backslash x_i y_i$	00	01	11	10
0		1		1
1	1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

$c_i \backslash x_i y_i$	00	01	11	10
0			1	
1	1	1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 

(c) Circuit

## Full Adder Example

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;
```

```
ENTITY fulladd IS  
    PORT ( x      : IN  
          y      : IN  
          cin    : IN  
          s      : OUT  
          cout   : OUT  
    );  
END fulladd ;
```

TIP: for architecture name for dataflow circuits  
use either "dataflow" or "entityname\_dataflow"

```
ARCHITECTURE fulladd_dataflow OF fulladd IS  
BEGIN  
    s <= x XOR y XOR cin ;  
    cout <= (x AND y) OR (cin AND x) OR (cin AND y) ;  
END fulladd_dataflow ;
```

13

## Logic Operators

- Logic operators

and	or	nand	nor	xor	not	xnor
-----	----	------	-----	-----	-----	------

- Logic operators precedence

Highest  
↓  
Lowest

			not			
and	or	nand	nor	xor	xnor	

only in VHDL-93  
and later

14

## No Implied Precedence

Wanted:  $y = ab + cd$

### Incorrect

`y <= a and b or c and d ;`

equivalent to

`y <= ((a and b) or c) and d ;`

equivalent to

`y = (ab + c)d`

### Correct

`y <= (a and b) or (c and d) ;`

15

## Concatenation

```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);
SIGNAL c, d, e: STD_LOGIC_VECTOR(7 DOWNTO 0);


a <= "0000";
b <= "1111";
c <= a & b;           -- c = "00001111"

d <= '0' & "0001111"; -- d <= "00001111"

e <= '0' & '0' & '0' & '0' & '1' & '1' &
    '1' & '1';       -- e <= "00001111"
```

16


## Rotations in VHDL

 

```
a_rotL <= a(2 downto 0) & a(3);
```

17

## Shifts in VHDL (zero-stuff)

 

```
a_shiftL <= a(2 downto 0) & '0';
```

Be careful if doing sign-extension

18

## Shifts in VHDL (using libraries)

- Using **std\_logic\_arith** package:
  - function SHL(ARG: UNSIGNED; COUNT: UNSIGNED) return UNSIGNED;
  - function SHL(ARG: SIGNED; COUNT: UNSIGNED) return SIGNED;
  - function SHR(ARG: UNSIGNED; COUNT: UNSIGNED) return UNSIGNED;
  - function SHR(ARG: SIGNED; COUNT: UNSIGNED) return SIGNED;
- Make sure your syntax is correct
- Recommend not using these functions, but "hard-wiring" the shifts as in previous examples

19

## Dataflow VHDL

### *Major instructions*

#### **Concurrent statements**


- concurrent signal assignment ( $\Leftarrow$ )
- **conditional concurrent signal assignment (when-else)**
- selected concurrent signal assignment (with-select-when)
- generate scheme for equations (for-generate)

20

## Conditional concurrent signal assignment
 
### When - Else

```
target_signal <= value1 when condition1 else  
                value2 when condition2 else  
                . . .  
                valueN-1 when conditionN-1 else  
                valueN;
```



21

## Operators

- Relational operators

=    /=    <    <=    >    >=

- Logic and relational operators precedence

Highest  
↓  
Lowest

=	/=	<	<=	>	>=
and	or	nand	nor	xor	xnor

not

22

## Priority of Logic and Relational Operators

compare `a = bc`

### Incorrect

... when `a = b and c` else ...

equivalent to

... when `(a = b) and c` else ...

### Correct


... when `a = (b and c)` else ...

23
 
## Tri-state Buffer – example

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY tri_state IS
    PORT ( ena:    IN STD_LOGIC;
          input:  IN STD_LOGIC_VECTOR(7 downto 0);
          output: OUT STD_LOGIC_VECTOR (7 DOWNT0 0)
        );
END tri_state;
ARCHITECTURE tri_state_dataflow OF tri_state IS
BEGIN
    output <= input WHEN (ena = '0') ELSE
              (OTHERS => 'Z');
END tri_state_dataflow;
```



OTHERS means all bits not directly specified,  
in this case all the bits.

24

## Dataflow VHDL

### *Major instructions*

#### Concurrent statements


- concurrent signal assignment ( $\Leftarrow$ )
- conditional concurrent signal assignment  
(when-else)
- **selected concurrent signal assignment**  
**(with-select-when)**
- generate scheme for equations  
(for-generate)

25

## Selected concurrent signal assignment
 
### *With –Select-When*

```
with choice_expression select  
  target_signal <= expression1 when choices_1,  
                    expression2 when choices_2,  
                    . . .  
                    expressionN when choices_N;
```



26

## Allowed formats of *choices\_k*

```
WHEN value
```

```
WHEN value_1 to value_2
```

```
WHEN value_1 | value_2 | .... | value N
```



this means boolean "or"

27


## Allowed formats of *choice\_k* - example

```
WITH sel SELECT  
  y <= a WHEN "000",  
        b WHEN "011" to "110",  
        c WHEN "001" | "111",  
        d WHEN OTHERS;
```

28

$\sum_{k=1}^n (m_k - 1)(m_k + 1) = \dots$

# MLU Example

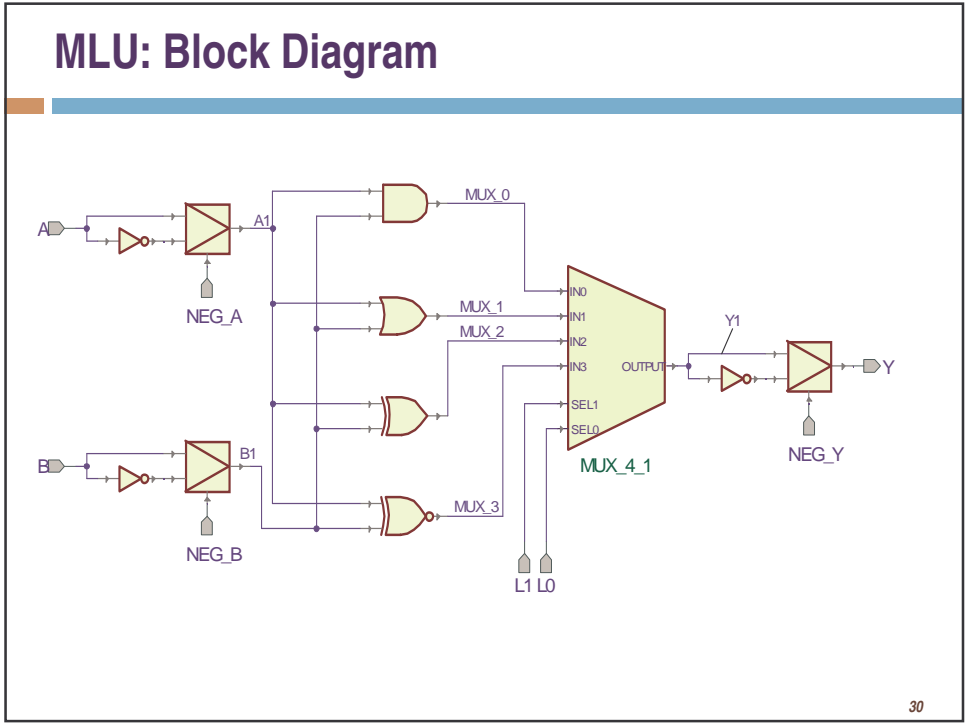

## MLU: Entity Declaration

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mlu IS
  PORT(
    NEG_A : IN STD_LOGIC;
    NEG_B : IN STD_LOGIC;
    NEG_Y : IN STD_LOGIC;
    A :    IN STD_LOGIC;
    B :    IN STD_LOGIC;
    L1 :   IN STD_LOGIC;
    L0 :   IN STD_LOGIC;
    Y :    OUT STD_LOGIC
  );
END mlu;
```

31

## MLU: Architecture Declarative Section

```
ARCHITECTURE mlu_dataflow OF mlu IS

  SIGNAL A1 : STD_LOGIC;
  SIGNAL B1 : STD_LOGIC;
  SIGNAL Y1 : STD_LOGIC;
  SIGNAL MUX_0 : STD_LOGIC;
  SIGNAL MUX_1 : STD_LOGIC;
  SIGNAL MUX_2 : STD_LOGIC;
  SIGNAL MUX_3 : STD_LOGIC;
  SIGNAL L : STD_LOGIC_VECTOR(1 DOWNTO 0);
```

32

## MLU - Architecture Body

```
BEGIN
  A1<= NOT A  WHEN (NEG_A='1') ELSE
        A;
  B1<= NOT B  WHEN (NEG_B='1') ELSE
        B;
  Y <= NOT Y1 WHEN (NEG_Y='1') ELSE
        Y1;

  MUX_0 <= A1 AND  B1;
  MUX_1 <= A1 OR   B1;
  MUX_2 <= A1 XOR  B1;
  MUX_3 <= A1 XNOR B1;

  L <= L1 & L0;

  with (L) select
    Y1 <= MUX_0 WHEN "00",
          MUX_1 WHEN "01",
          MUX_2 WHEN "10",
          MUX_3 WHEN OTHERS;

END mlu_dataflow;
```

33

## Data-flow VHDL

### *Major instructions*

#### Concurrent statements

- concurrent signal assignment ( $\Leftarrow$ )
- conditional concurrent signal assignment  
(when-else)
- selected concurrent signal assignment  
(with-select-when)
- **generate scheme for equations**  
(for-generate)

34

## For Generate Statement

*For - Generate*


```
label: FOR identifier IN range GENERATE  
      BEGIN  
        {Concurrent Statements}  
      END GENERATE [label];
```

35

## PARITY Example

36

## PARITY: Block Diagram

 

37


## PARITY: Entity Declaration

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY parity IS
    PORT(
        parity_in    : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
        parity_out   : OUT STD_LOGIC
    );
END parity;
```

38

## PARITY: Block Diagram

 

39

## PARITY: Architecture

```
ARCHITECTURE parity_dataflow OF parity IS

    SIGNAL xor_out: std_logic_vector (6 downto 1);


BEGIN

    xor_out(1) <= parity_in(0) XOR parity_in(1);
    xor_out(2) <= xor_out(1) XOR parity_in(2);
    xor_out(3) <= xor_out(2) XOR parity_in(3);
    xor_out(4) <= xor_out(3) XOR parity_in(4);
    xor_out(5) <= xor_out(4) XOR parity_in(5);
    xor_out(6) <= xor_out(5) XOR parity_in(6);
    parity_out <= xor_out(6) XOR parity_in(7);

END parity_dataflow;
```

40

## PARITY: Block Diagram (2)

 

41

## PARITY: Architecture

```
ARCHITECTURE parity_dataflow OF parity IS
```

```
SIGNAL xor_out: STD_LOGIC_VECTOR (7 downto 0);
```

```
BEGIN
```

```
    xor_out(0) <= parity_in(0);  
    xor_out(1) <= xor_out(0) XOR parity_in(1);  
    xor_out(2) <= xor_out(1) XOR parity_in(2);  
    xor_out(3) <= xor_out(2) XOR parity_in(3);  
    xor_out(4) <= xor_out(3) XOR parity_in(4);  
    xor_out(5) <= xor_out(4) XOR parity_in(5);  
    xor_out(6) <= xor_out(5) XOR parity_in(6);  
    xor_out(7) <= xor_out(6) XOR parity_in(7);  
    parity_out <= xor_out(7);
```

```
END parity_dataflow;
```

42

## PARITY: Architecture (2)

```
ARCHITECTURE parity_dataflow OF parity IS
SIGNAL xor_out: STD_LOGIC_VECTOR (7 DOWNTO 0);

BEGIN

    xor_out(0) <= parity_in(0);

    G2: FOR i IN 1 TO 7 GENERATE
        xor_out(i) <= xor_out(i-1) XOR parity_in(i);
    END GENERATE;

    parity_out <= xor_out(7);

END parity_dataflow;
```

43

## Combinational Logic Synthesis for Beginners

44

## Simple Rules

For combinational logic,  
use only concurrent statements

- concurrent signal assignment ( $\Leftarrow$ )
- conditional concurrent signal assignment  
(when-else)
- selected concurrent signal assignment  
(with-select-when)
- generate scheme for equations  
(for-generate)

45

## Simple Rules

- For circuits composed of:
  - simple logic operations (logic gates)
  - simple arithmetic operations (addition, subtraction, multiplication)
  - shifts/rotations by a constant
- Use
  - concurrent signal assignment ( $\Leftarrow$ )

46

## Simple Rules

- For circuits composed of
  - multiplexers
  - decoders, encoders
  - tri-state buffers
- Use:
  - conditional concurrent signal assignment (when-else)
  - selected concurrent signal assignment (with-select-when)

47

## Left versus Right Side

### Left side

<=

### Right side

<= when-else

with-select <=

- Internal signals (defined in a given architecture)
- Ports of the mode
  - **out**
  - inout
  - buffer (don't recommend using buffer in this class)

Expressions including:

- Internal signals (defined in a given architecture)
- Ports of the mode
  - **in**
  - inout
  - buffer

48

## Signed and Unsigned Arithmetic

49

### Arithmetic operations

Synthesizable arithmetic operations:

- Addition: +
- Subtraction: -
- Comparisons: >, >=, <, <=
- Multiplication: \*
- Division by a power of 2: /2\*\*6  
(equivalent to right shift)
- Shifts by a constant: SHL, SHR

50

## Arithmetic operations

The result of synthesis of an arithmetic operation is a

- combinational circuit
- without pipelining

The exact internal **architecture** used (and thus delay and area of the circuit) **may depend** on the **timing constraints** specified during synthesis (e.g., the requested maximum clock frequency).

51

## IEEE Packages for Arithmetic

- `std_logic_1164`
  - Official IEEE standard
  - Defines **std\_logic** and **std\_logic\_vector**
    - example: `std_logic_vector(7 downto 0)`
  - These are for logic operations (AND, OR) not for arithmetic operations (+, \*)
- `std_logic_arith`
  - Not official IEEE standard (created by Synopsys)
  - Defines **unsigned** and **signed** data types, example: `unsigned(7 downto 0)`
  - These are for arithmetic (+,\*) not for logic (AND, OR)
- `std_logic_unsigned`
  - Not official IEEE standard (created by Synopsys)
  - Including this library tells compiler to treat **std\_logic\_vector** like **unsigned** type in certain cases
    - For example, can perform addition on `std_logic_vector`
  - Used as a helper to avoid explicit conversion functions
- `std_logic_signed`
  - Not official IEEE standard (created by Synopsys)
  - Same functionality as `std_logic_unsigned` except tells compiler to treat **std\_logic\_vector** like **signed** type in certain cases
  - **Do not use both `std_logic_unsigned` and `std_logic_signed` at the same time!**
    - If need to do both signed and unsigned arithmetic in same entity, do not use `std_logic_unsigned` or `std_logic_signed` packages → do all conversions explicitly

52

## Library inclusion

- When dealing with unsigned arithmetic use:

```
LIBRARY IEEE;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all; ← needed for using unsigned data type
USE ieee.std_logic_unsigned.all;
```

- When dealing with signed arithmetic use:

```
LIBRARY IEEE;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all; ← need for using signed data type
USE ieee.std_logic_signed.all;
```

- When dealing with both unsigned and signed arithmetic use:

```
LIBRARY IEEE;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;
```

→ Then do all type conversions explicitly

53

## History: std\_logic\_arith versus numeric\_std

- History
  - Package std\_logic\_arith created by Synopsys as a stop-gap measure
  - Eventually, the IEEE created their own official “version” of std\_logic\_arith called numeric\_std
- numeric\_std
  - Official IEEE standard
  - Defines **unsigned** and **signed**
  - These are for arithmetic (+,\*) not for logic (AND, OR)
    - example: unsigned(7 downto 0)
  - **Use either numeric\_std or std\_logic\_arith, not both!**
- When dealing with unsigned and/or signed types using numeric\_std, use:

```
LIBRARY IEEE;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;
```
- Since different CAD vendors may implement std\_logic\_arith differently, you can use numeric\_std to be safe
  - However ... many legacy designs and companies use std\_logic\_arith in combination with std\_logic\_unsigned or std\_logic\_signed
  - **Examples in class and in exams will use std\_logic\_arith with std\_logic\_unsigned/signed, and not use numeric\_std**
  - If you use numeric\_std, make sure to declare it properly so all code compiles

54

## Example: std\_logic\_arith versus numeric\_std

### UNSIGNED ADDER WITH NO CARRYOUT

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.std_logic_arith.all; -- not needed but keep for style
use IEEE.std_logic_unsigned.all;
entity adder is
port(
  a : in STD_LOGIC_VECTOR(2 downto 0);
  b : in STD_LOGIC_VECTOR(2 downto 0);
  c : out STD_LOGIC_VECTOR(2 downto 0) );
end adder;

architecture adder_arch of adder is
begin
  c <= a + b;
end adder_arch;

```

Tells compiler to  
treat std\_logic\_vector  
like unsigned type

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.numeric_std.all;
entity adder is
port(
  a : in STD_LOGIC_VECTOR(2 downto 0);
  b : in STD_LOGIC_VECTOR(2 downto 0);
  c : out STD_LOGIC_VECTOR(2 downto 0) );
end adder;

architecture adder_arch of adder is
begin
  c <= std_logic_vector(unsigned(a) + unsigned(b));
end adder_arch;

```

55

## Conversion functions

		numeric_std	std_logic_arith
<b>Type Conversion</b>			
std_logic_vector	-> unsigned	unsigned (arg)	unsigned (arg)
std_logic_vector	-> signed	signed (arg)	signed (arg)
unsigned	-> std_logic_vector	std_logic_vector (arg)	std_logic_vector (arg)
signed	-> std_logic_vector	std_logic_vector (arg)	std_logic_vector (arg)
integer	-> unsigned	to_unsigned (arg, size)	conv_unsigned (arg, size)
integer	-> signed	to_signed (arg, size)	conv_signed (arg, size)
unsigned	-> integer	to_integer (arg)	conv_integer (arg)
signed	-> integer	to_integer (arg)	conv_integer (arg)
integer	-> std_logic_vector	integer -> unsigned/signed -> std_logic_vector	
std_logic_vector	-> integer	std_logic_vector -> unsigned/signed -> integer	
unsigned + unsigned	-> std_logic_vector	std_logic_vector (arg1 + arg2)	arg1 + arg2
signed + signed	-> std_logic_vector	std_logic_vector (arg1 + arg2)	arg1 + arg2
<b>Resizing</b>			
unsigned		resize (arg, size)	conv_unsigned (arg, size)
signed		resize (arg, size)	conv_signed (arg, size)

From: <http://dz.ee.ethz.ch/support/ic/vhdl/vhdlsources.en.html>

56

## More information?

- Go to:
  - <http://dz.ee.ethz.ch/support/ic/vhdl/vhdlsources.en.html>
- Download
  - std\_logic\_arith.vhd
  - std\_logic\_unsigned.vhd
  - std\_logic\_signed.vhd
  - numeric\_std
  - ...and compare them

57

## Unsigned and Signed Numbers

- N-bit unsigned number: unsigned(N-1 downto 0)
  - Has a decimal range of 0 to  $2^N-1$ 
    - Example: unsigned(7 downto 0) has a decimal range 0 to 255
- N-bit signed number (two's complement) number: signed(N-1 downto 0)
  - Has a decimal range of  $-2^{N-1}$  to  $2^{N-1}-1$ 
    - Asymmetric range due to non-redundant representation of 0
    - Example: signed(7 downto 0) has a decimal range -128 to 127
  - MSB indicates sign
    - '0' in MSB means non-negative (0 or positive)
    - '1' in MSB means negative
  - To negate a two's complement number: invert all bits, add '1' to LSB
    - $010 = 2$
    - to get -2, invert then add '1':  $101 + 1 = 110$
  - Sign extension does not affect value
    - Example: 010 and 00010 both represent decimal 2
    - Example: 110 and 11110 both represent decimal -2

58

## Unsigned versus Signed

Binary	Unsigned value (decimal)	Signed value (decimal)
0000	0 (zero)	0 (zero)
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7 (largest positive value)	7 (largest positive value)
1000	8	-8 (largest negative value)
1001	9	-7
1010	10	-6
1011	11	-5
1100	12	-4
1101	13	-3
1110	14	-2
1111	15 (largest positive value)	-1 (smallest negative value)

59

## Addition of Unsigned Numbers

A (2 bits)	B (2 bits)	SUM = A + B DECIMAL	SUM BINARY	SUM and CARRYOUT BINARY
00	00	0 + 0 = 0	00	000
01	00	1 + 0 = 1	01	001
10	00	2 + 0 = 2	10	010
11	00	3 + 0 = 3	11	011
00	01	0 + 1 = 1	01	001
01	01	1 + 1 = 2	10	010
10	01	2 + 1 = 3	11	011
11	01	3 + 1 = 4	00	100
00	10	0 + 2 = 2	10	010
01	10	1 + 2 = 3	11	011
10	10	2 + 2 = 4	00	100
11	10	3 + 2 = 5	01	101
00	11	0 + 3 = 3	11	011
01	11	1 + 3 = 4	00	100
10	11	2 + 3 = 5	01	101
11	11	3 + 3 = 6	10	110

RED indicates loss of information (i.e. incorrect answer) if carryout not kept and just tried to zero-pad SUM

60

## Unsigned Addition: No Carryout

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;
use IEEE.STD_LOGIC_UNSIGNED.all;

entity adder_unsigned is
  port(
    a : in STD_LOGIC_VECTOR(1 downto 0);
    b : in STD_LOGIC_VECTOR(1 downto 0);
    sum : out STD_LOGIC_VECTOR(1 downto 0));
end adder_unsigned;

architecture dataflow of adder_unsigned is

begin
  sum <= a + b;
end dataflow;
```

61

## Unsigned Addition: With Carryout

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;
use IEEE.STD_LOGIC_UNSIGNED.all;

entity adder_unsigned_carryout is
  port(
    a : in STD_LOGIC_VECTOR(1 downto 0);
    b : in STD_LOGIC_VECTOR(1 downto 0);
    sum : out STD_LOGIC_VECTOR(1 downto 0);
    cout : out STD_LOGIC );
end adder_unsigned_carryout;

architecture dataflow of adder_unsigned_carryout is
  signal tempsum : std_logic_vector(2 downto 0);
begin
  tempsum <= ('0' & a) + ('0' & b); -- pad with '0' before addition
  sum <= tempsum(1 downto 0);
  cout <= tempsum(2);
end dataflow;
```

62

## Addition of Signed Numbers

A (2 bits)	B (2 bits)	SUM = A + B DECIMAL	SUM BINARY	SUM and CARRYOUT BINARY
00	00	0 + 0 = 0	00	000
01	00	1 + 0 = 1	01	001
10	00	-2 + 0 = -2	10	110
11	00	-1 + 0 = -1	11	111
00	01	0 + 1 = 1	01	001
01	01	1 + 1 = 2	10	010
10	01	-2 + 1 = -1	11	111
11	01	-1 + 1 = 0	00	000
00	10	0 + -2 = -2	10	110
01	10	1 + -2 = -1	11	111
10	10	-2 + -2 = -4	00	100
11	10	-1 + -2 = -3	01	101
00	11	0 + -1 = -1	11	111
01	11	1 + -1 = 0	00	000
10	11	-2 + -1 = -3	01	101
11	11	-1 + -1 = -2	10	110

RED indicates loss of information (i.e. incorrect answer) if carryout not kept and just tried to sign-extend SUM

63

## Signed Addition: No Carryout

```

library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;
use IEEE.STD_LOGIC_SIGNED.all;

entity adder_signed is
    port(
        a : in STD_LOGIC_VECTOR(1 downto 0);
        b : in STD_LOGIC_VECTOR(1 downto 0);
        sum : out STD_LOGIC_VECTOR(1 downto 0));
end adder_signed;

architecture dataflow of adder_signed is

begin
    sum <= a + b;
end dataflow;
    
```

64

## Signed Addition: With Carryout

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.STD_LOGIC_ARITH.all;
use IEEE.STD_LOGIC_SIGNED.all;

entity adder_signed_carryout is
    port(
        a : in STD_LOGIC_VECTOR(1 downto 0);
        b : in STD_LOGIC_VECTOR(1 downto 0);
        sum : out STD_LOGIC_VECTOR(1 downto 0);
        cout : out STD_LOGIC );
end adder_signed_carryout;

architecture dataflow of adder_signed_carryout is
    signal tempsum : std_logic_vector(2 downto 0);
begin
    tempsum <= (a(1) & a) + (b(1) & b); -- sign extend BEFORE addition, very important
    sum <= tempsum(1 downto 0);
    cout <= tempsum(2);
end dataflow;
```

65

## Testbench: Signed Addition with Carry Out

```
library ieee;
use ieee.std_logic_signed.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_1164.all;

entity adder_signed_carryout_tb is
end adder_signed_carryout_tb;

architecture TB_ARCHITECTURE of adder_signed_carryout_tb is
    component adder_signed_carryout
        port(
            a : in std_logic_vector(1 downto 0);
            b : in std_logic_vector(1 downto 0);
            sum : out std_logic_vector(1 downto 0);
            cout : out std_logic );
        end component;
    signal a : std_logic_vector(1 downto 0) := "00";
    signal b : std_logic_vector(1 downto 0) := "00";
    signal sum : std_logic_vector(1 downto 0);
    signal cout : std_logic;
```


66

## Tesbench cont'd

```
begin
    UUT : adder_signed_carryout
        port map (
            a => a,
            b => b,
            sum => sum,
            cout => cout
        );
    process
    begin
        for i in 0 to 3 loop
            for j in 0 to 3 loop
                wait for 10 ns;
                b <= b + 1;
            end loop;
            a <= a + 1;
        end loop;
        wait;
    end process;
end TB_ARCHITECTURE;
```

67

## Waveform

 

68

## Multiplication

- N-bit unsigned number x M-bit unsigned number results in N+M bit unsigned number
  - Example: 3 bits x 4 bits = 7 bits
  - 111 (7) x 1111 (15) = 1101001 (105) → most positive x most positive needs 7 bits
- N-bit signed number x M-bit signed number results in N+M bit unsigned number
  - Example: 3 bits x 4 bits
  - 100 (-4) x 1000 (-8) = 0100000 (+32) → most negative x most negative needs 7 bits (this is the only scenario which requires the full output range)
  - 100 (-4) x 0111 (7) = [1]100100 (-28) → most negative x most positive needs 6 bits, [ ] indicates not necessary
  - 011 (3) x 0111 (7) = [0]010101 (21) → most positive x most positive needs 6 bits
  - 011 (3) x 1000 (-8) = [1]101000 (-24) → most positive x most negative needs 6 bits

69

## Multiplication of signed and unsigned numbers (1)

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_arith.all;

entity multiply is
  port(
    a : in STD_LOGIC_VECTOR(15 downto 0);
    b : in STD_LOGIC_VECTOR(7 downto 0);
    cu : out STD_LOGIC_VECTOR(23 downto 0);
    cs : out STD_LOGIC_VECTOR(23 downto 0)
  );
end multiply;

architecture dataflow of multiply is

  SIGNAL sa: SIGNED(15 downto 0);
  SIGNAL sb: SIGNED(7 downto 0);
  SIGNAL sres: SIGNED(23 downto 0);

  SIGNAL ua: UNSIGNED(15 downto 0);
  SIGNAL ub: UNSIGNED(7 downto 0);
  SIGNAL ures: UNSIGNED(23 downto 0);
```

Since using both signed and unsigned data types, don't use std\_logic\_unsigned/signed. Do all conversions by hand.

70

## Multiplication of signed and unsigned numbers (2)

```
begin
-- signed multiplication
sa <= SIGNED(a);
sb <= SIGNED(b);
sres <= sa * sb;
cs <= STD_LOGIC_VECTOR(sres);

-- unsigned multiplication
ua <= UNSIGNED(a);
ub <= UNSIGNED(b);
ures <= ua * ub;
cu <= STD_LOGIC_VECTOR(ures);

end dataflow;
```

71

## Integer Types

Operations on signals (variables)  
of the integer types:

**INTEGER, NATURAL,**

and their subtypes, such as

TYPE day\_of\_month IS **RANGE 0 TO 31;**

are synthesizable in the range

$-(2^{31}-1) .. 2^{31} - 1$  for INTEGERS and their subtypes

$0 .. 2^{31} - 1$  for NATURALS and their subtypes

72

## Integer Types cont'd

Operations on signals (variables)  
of the integer types:

**INTEGER, NATURAL,**

are less flexible and more difficult to control  
than operations on signals (variables) of the type

**STD\_LOGIC\_VECTOR**

**UNSIGNED**

**SIGNED,** and thus

are recommended to be avoided by beginners unless necessary.