
 


ECE680: Physical VLSI Design

Chapter V


Implementation Strategies for Digital ICs Part 2: Issues of Logic Gates

Clock Overlap and Race Condition

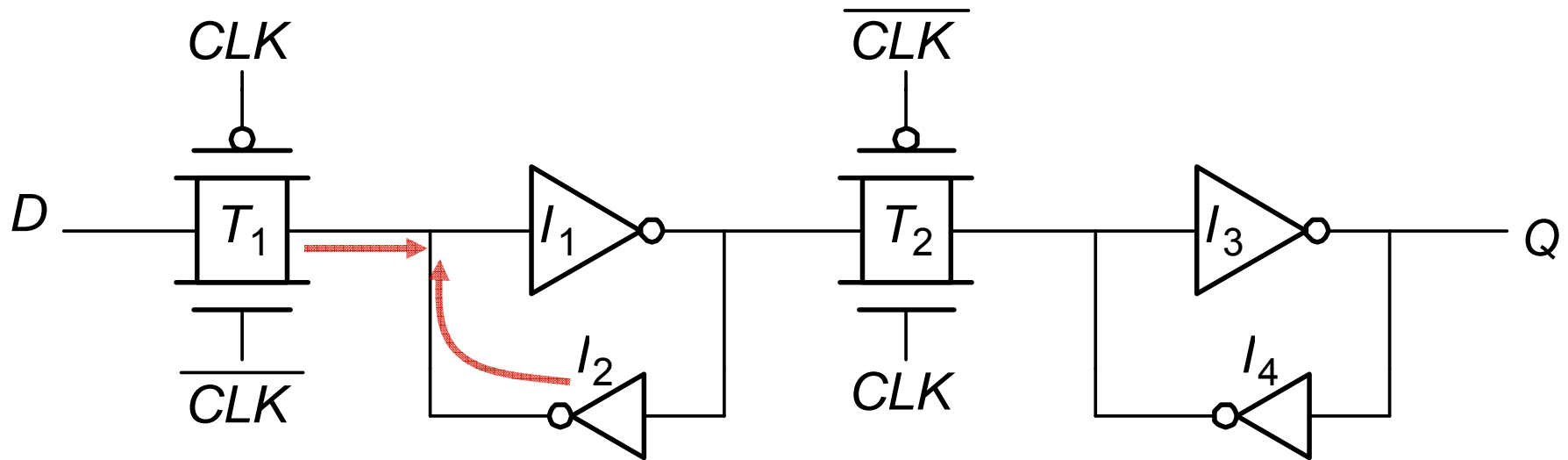


Overlapping clock pairs (1,1) and (0,0)



Avoid Clock Overlap

 

 nMOS FF with nonoveralp (high) clocks PHI1 and PHI2



Avoid Clock Overlap

 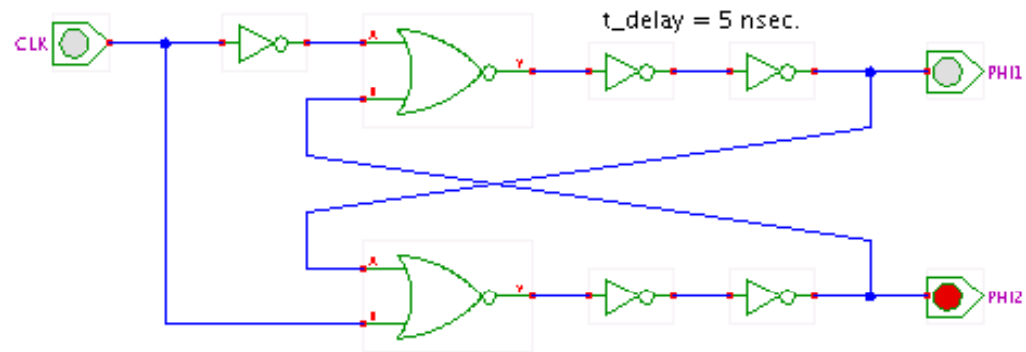


Avoid Clock Overlap

Insensitive to CLK and \overline{CLK} overlap

» Prevents a change on D from affecting Q during overlap



Clock CMOS

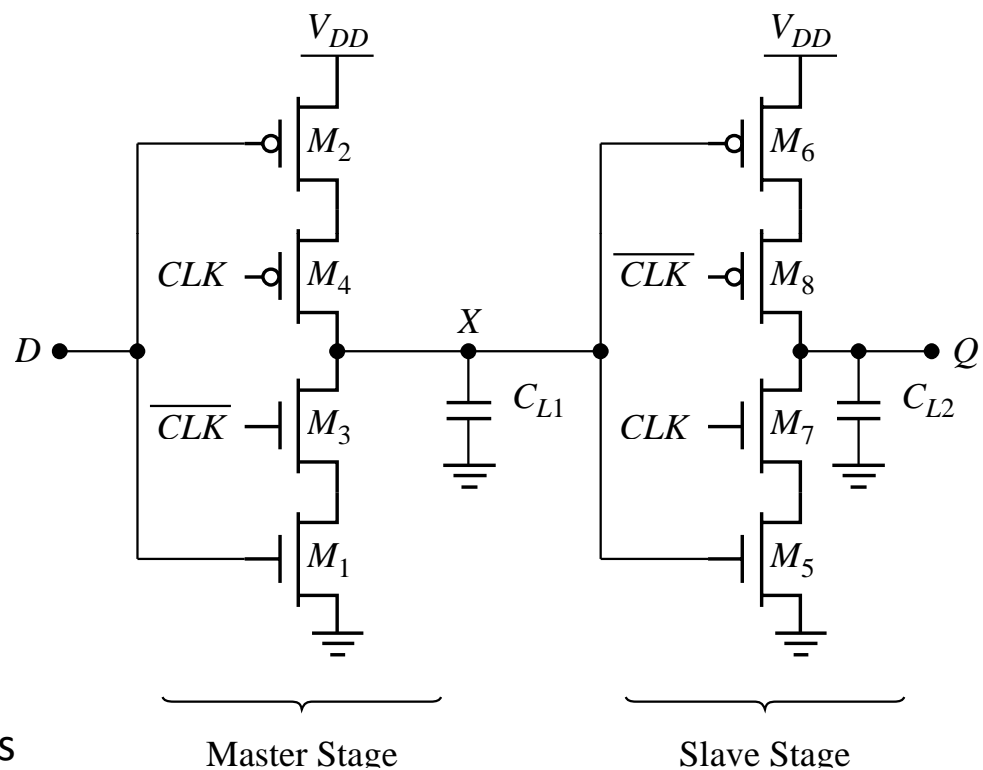

Disadvantages

- Short-Circuit currents destroy charge stored at X and Q
- For correct operation, ensure that $t_{\text{riseCLK}} < 5 t_{c-q}$

  Avoid Clock Overlap by using static SR FF





S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State


Avoid Clock Overlap by using static SR FF

Cross-coupled NANDs

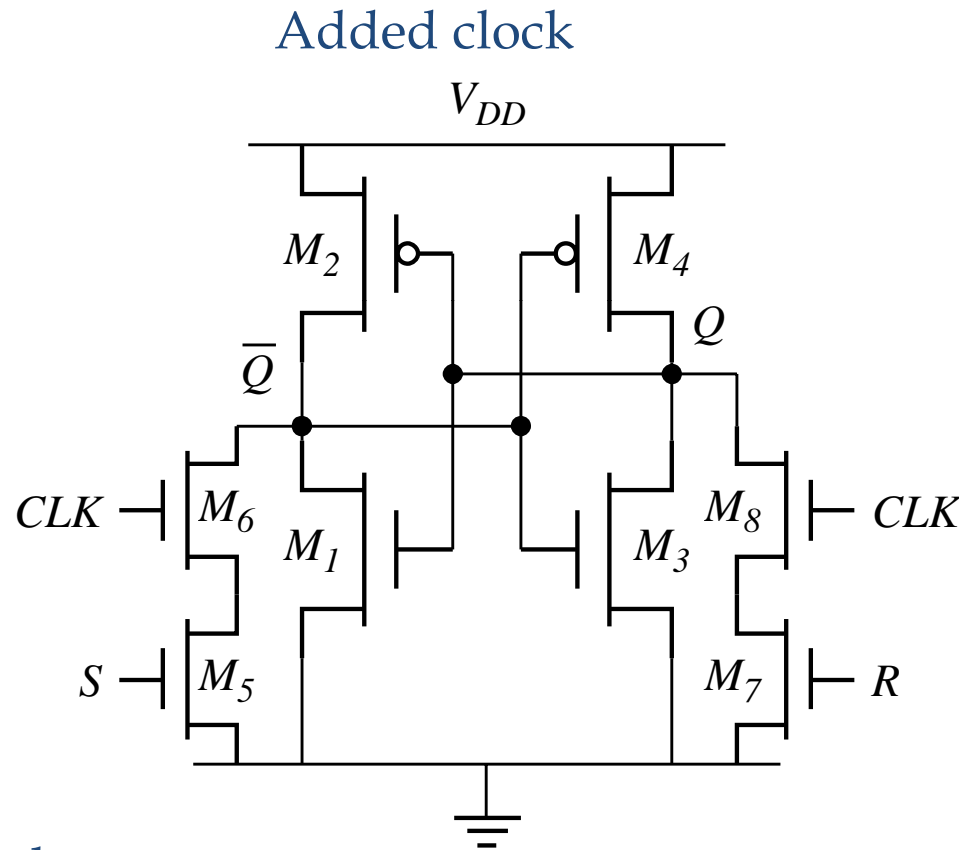 


This is not used in datapaths any more,
but is a basic building memory cell

 
Non-Bistable Sequential Circuits— Schmitt Trigger



 
- VTC with hysteresis
- Restores signal slopes



Noise Suppression using Schmitt Trigger

 


CMOS Schmitt Trigger

 


Moves switching threshold of the first inverter

Schmitt Trigger Simulated VTC

 

 Voltage-transfer characteristics with hysteresis.



The effect of varying the ratio of the PMOS device M_4 . The width is $k \cdot 0.5 \mu m$.

